




## Logic Project Report

Sunday 4-6		
ID	Name	Tasks
1190419	Zyad Khaled Salah	4-Bit Adder Multiplier
1190384	Moaz Ahmed Abomousa	Negative Subtract Not
1190477	Omar Mohamed Faheem	Shift Left Shift Right Move
1190423	Nourhan Ahmed Helmy	And Or Xor


## Block Diagrams & No. of Gates

### 1-Move:

 

➤ Gates: 0

### 2-Negative:

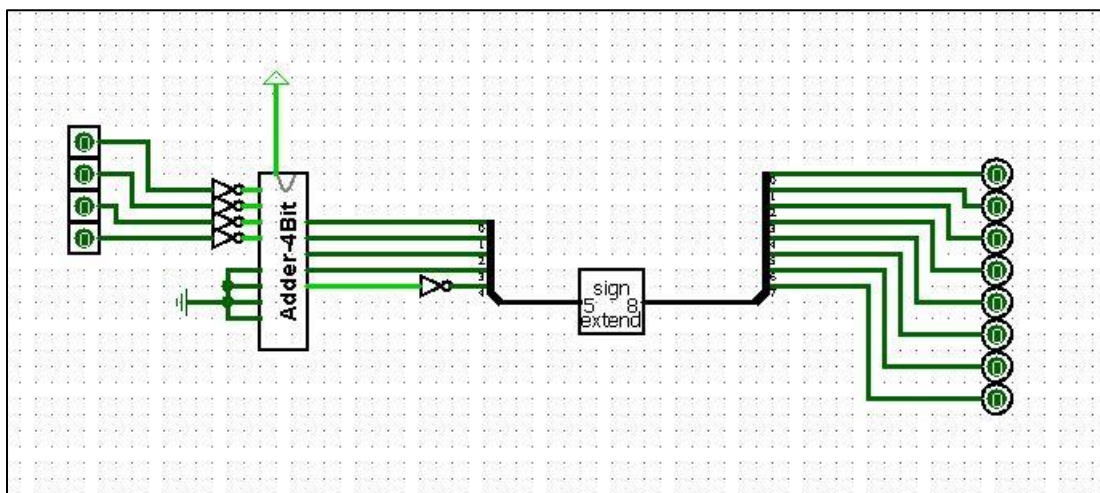


➤ Gates:

Gate	Number of occurrences
2-AND	8
2-OR	4
XOR	8
NOT	5
Total	225





### 3-Bit Adder:

#### Half Adder:

 

#### Full Adder:

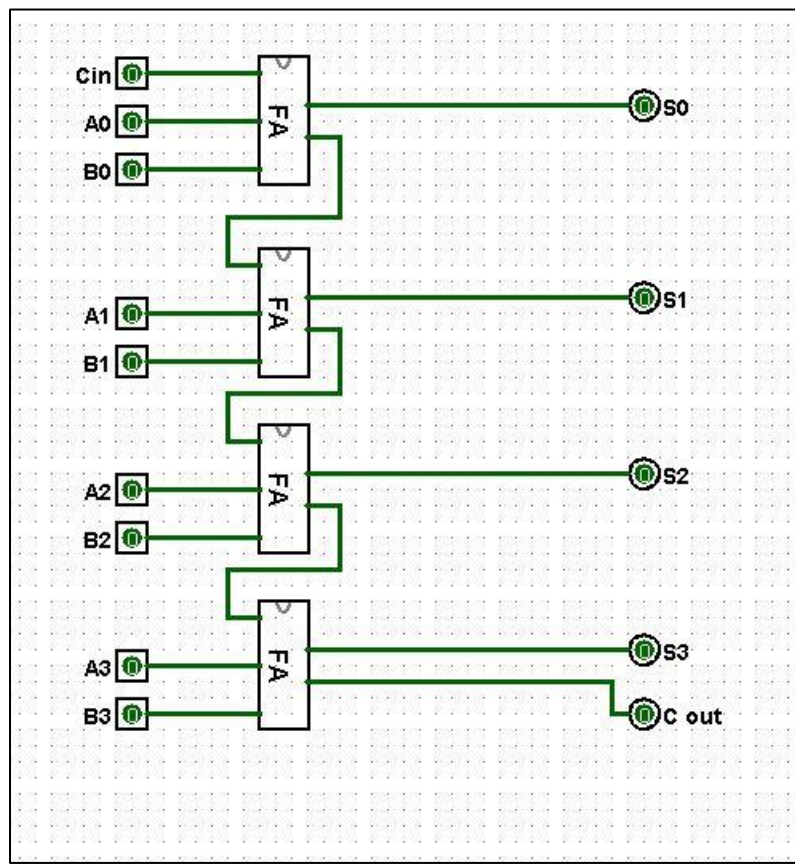 




➤ Gates:

Gate	Number of occurrences
2-AND	8
2-OR	4
XOR	8
Total	20

**4-Subtractor:**

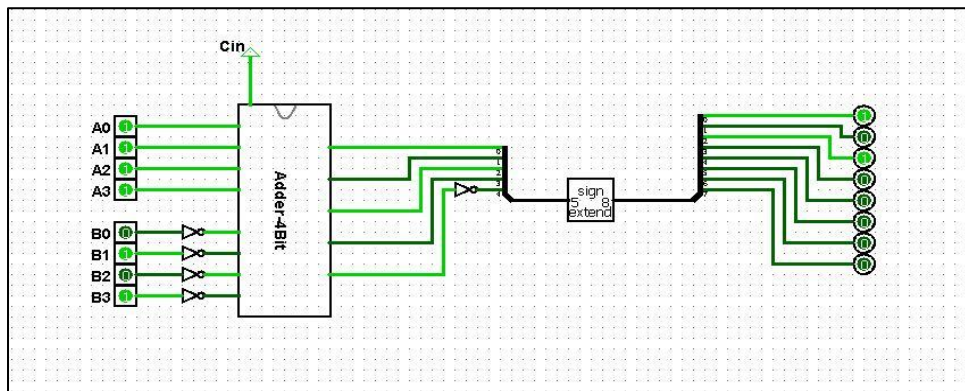


➤ Gates:

Gate	Number of occurrences
2-AND	8
2-OR	4
XOR	8
NOT	5
Total	225




### 5-Multiplier:

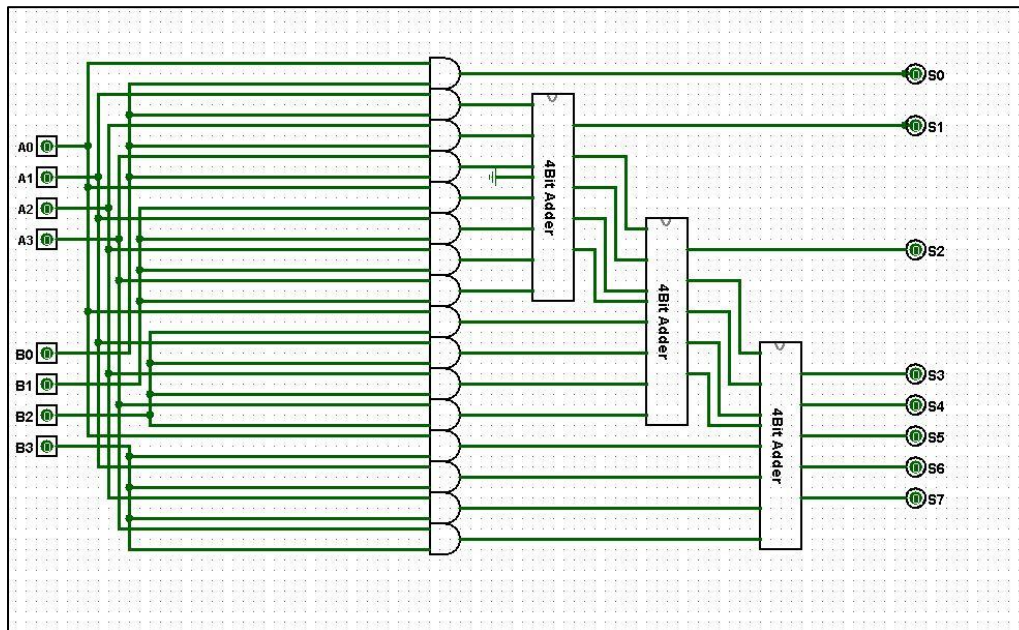

#### ➤ Gates:

Gate	Number of occurrences
2-AND	40
2-OR	12
XOR	24
Total	76

### 6-Not:

 




➤ Gates:

Gate	Number of occurrences
NOT	8
Total	8


7-And:

 

➤ Gates:

Gate	Number of occurrences
AND	1
Total	1

8-Or:

 


➤ Gates:

Gate	Number of occurrences
OR	1
Total	1




### 9-Xor:

 



#### ➤ Gates:

Gate	Number of occurrences
XOR	1
Total	1

### 10-Shift Left:

 




 
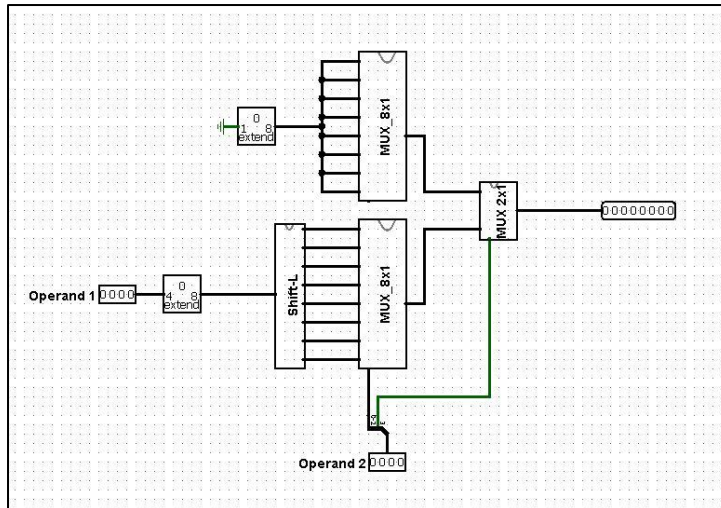


➤ Gates:

Gate	Number of occurrences
2-AND	30
2-OR	15
NOT	15
Total	60



## 11-Shift Right:

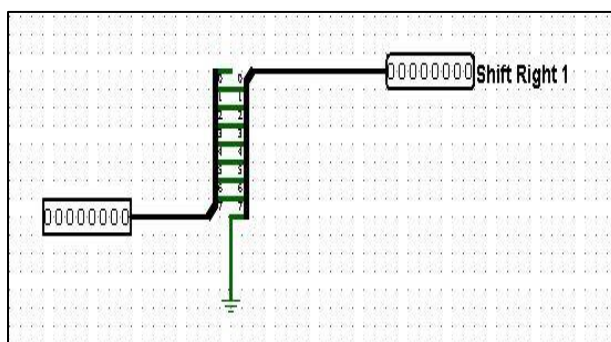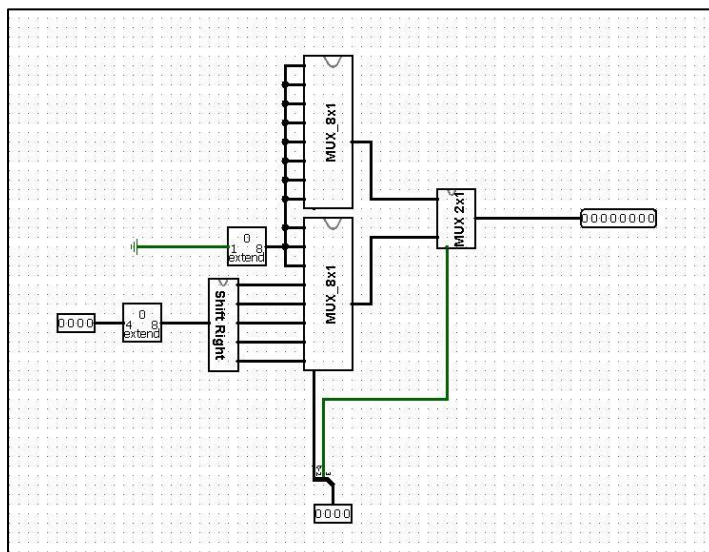 

## ➤ Gates:



Gate	Number of occurrences
2-AND	30
2-OR	15
NOT	15
Total	60

### Final Circuit Presentation

